

Project 1: Report

Single Cycle Implementation:

File Name: Alu.v

- Encodes ALU
 - Has three inputs, A, B, and Control
 - Outputs result or zero
 - Has add and subtract function

File Name: Alu_Control_Unit.v

- Immediate
 - Inputs an immediate value (integer)
 - Outputs Sign Immediate

File Name: Control_Unit.v

- Sets opcode values
 - Outputs ALUOp, MemWrite, RegWrite, RegDst, MemtoReg, ALUSrc, Branch, and Jump
 - Inputs opcode

File Name: Data_Memory.v

- Reads and writes to data memory
 - Inputs A, WD, WE, clk, rst_n
 - Outputs RD
 - Writes or reads to an address in memory

File Name: Imm_Sign_Extend.v

- Assigns new sign extension
 - Inputs an immediate value (integer)
 - Outputs Sign Immediate

File Name: Instruction_Memory.v

- Instruction of memory
 - Inputs A
 - Outputs RD
 - Read instruction of memory.

File Name: MIP_Single_Cycle.v

- Single Cycle
 - Inputs A
 - Outputs RD
 - Contains all the wires for instructions

File Name: PC.v

- PC counter
 - Inputs clk, rst_n, immediate, jump low 26 bits, PCSrc,
 - Outputs the zero from the ALU as input and PC for the output.

File Name: Register_Files.v

- encloses all the registers that are independent of the processor which is to perform read and write operations which is done by getting the input and assigning whether its for reading or writing
 - Input A1,A2,A3,RegWrite,WD3
 - Output RD1,RD2
 - Sets RegWrite to 1 when lw Instr is executed

File Name: tb_SingleCycle.v

- Connects all the files and assigns dump files where gtkwave will use to form waves
 - Also controls the clock cycle

File Name: Mips_wave.vcd

- Dump file for tb_SingleCycle

File Name: memfile.dat

- Data input

Pipeline:

File Name: Alu.v

- ALU with pipeline support
 - Has inputs rst_n (system clock), SignImm, ALUControl, ALUSrc, ForwardAE, ForwardBE, ResultW, ALUOutM, RD1E, RD2E
 - Outputs SRCB_Foward, ALUOut, and Zero
 - Can forward data or stall

File Name: ALU_Control_Unit.v

- ALU control unit
 - Has inputs Funct and ALUOp
 - Outputs ALUControl
 - Receives ALU opcode from control unit and converts it to ALU

File Name: Branch_Unit.v

- Branch Unit
 - Has inputs BranchD, SignImm, PCPlus4D, RD1, RD2, ALUOutM, ForwardAD, and ForwardBD
 - Outputs PCBranchD and PCSrcD
 - Allows hardware to branch and jump to other lines of code

File Name: Control_Unit.v

- Sets opcode values
 - Inputs opcode and rst_n (system clock)
 - Outputs ALUOp, MemWrite, RegWrite, RegDst, MemtoReg, ALUSrc, Branch, and Jump

File Name: Data_Memory.v

- Reads and writes to data memory
 - Inputs A, WD, WE
 - Outputs RD
 - Writes or reads to an address in memory

File Name: EX_MEM_Register.v

- Gives memory address to read and write to
 - Has inputs clk, rst_n, ALUOut, WriteDataE, WriteRegE, Zero, RegWriteE, MemtoRegE, MemWriteE
 - Outputs ALUOutM, WriteDataM, WriteRegM, ZeroM, RegWriteM, MemtoRegM, MemWriteM
 - Third stage of clock cycle to execute

File Name: Forward_Unit.v

- Solve the data hazards
 - Input rst_n, RsE, RtE, RsD, RtD, WriteRegM, WriteRegW, RegWriteM, RegWriteW

- First, if hazard in EX/MEM.RegisterRd = ID/EX.RegisterRs then the first ALU Operand come from last ALU calculate result.
- Second, the hazard is happened in MEM/WB.RegisterRd = ID/EX.RegisterRt then he first ALU Operand come from last ALU calculate result or Memory data.
- Last, addi Hazard: EX.MEM.RegisterRd
- Output ForwardAE, ForwardBE, ForwardAD, ForwardBD

File Name: ID_EX_Resgister

- Instruction decode and executive
 - Input: clk, rst_n, RD1, RD2, Rt, Rs, Rd, SignImm, PCPlus4D, ALUControlD, FlushE, RegWriteD, MemtoRegD, MemWriteD, RegDstD, ALUSrcD,
 - Output: RD1E, RD2E, RtE ,RsE, RdE ,SignImmE, PCPlus4E,RegWriteE, MemtoRegE, MemWriteE, RegDstE, ALUSrcE, ALUControlE
 - the register numbers to read the two registers.

File Name: IF_ID_Register.v

- Instruction Fetch and Instruction decode
 - Input clk, rst_n, RD1, RD2, Rt, Rs, Rd, SignImm, PCPlus4D
 - Output PCPlus4D,InstrD

File Name: Imm_Sign_Extend.v

- Assigns new sign extension
 - Input Immediate
 - Output SignImm
 - Sign Extend immediate

File Name: Instruction_Memory.v

- Instruction of memory
 - Inputs A
 - Outputs RD
 - Read instruction of memory.

File Name: PC.v

- PC counter
 - Inputs clk, rst_n, PCSrcD, StallF, PCBranchD, jumpD, InstrD_Low25Bit
 - Outputs the zero from the ALU as input and PC for the output

File Name: Register_Files.v

- encloses all the registers that are independent of the processor which is to perform read and write operations which is done by getting the input and assigning whether its for reading or writing
 - Input A1, A2, A3, RegWrite, WD3
 - Output RD1,RD2
 - Sets RegWrite to 1 when lw Instr is executed

File Name: MIPS_Pipeline.v

- Contains all the wire and is what set everything for every instruction
 - Input: clock, rest_n

File Name: tb_MIPS_Pipeline.v

- Connects all the files and assigns dump files where gtkwave will use to form waves
 - Also controls the clock cycle

File Name: Mips_wave.vcd

- Dump file for tb_MIPS_Pipeline

File Name: memfile.dat

- Data input

File Name: Stall_Unit.v

- Hazard fix for Load Use Data and it initiates a stall
 - Input: clock, rest_n, RsD, RtD, RtE, WriteRegE, WriteRegM, RegWriteE, MemtoRegE, MemtoRegM, BranchD
 - Output: FlushE, StallD, StallF